Computer architecture

Hardware abstraction



Software abstraction






Hardware abstraction

Transistor is the basic element of computer. It can turn a current on and off.


Logic gate (And, ...) is built from transistors.

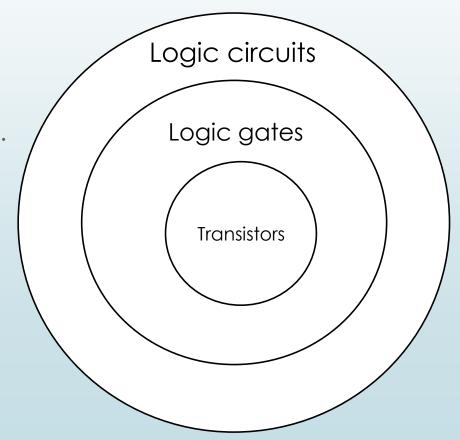Logic circuit (Adder, ...) is built from logic gates.




Transistor

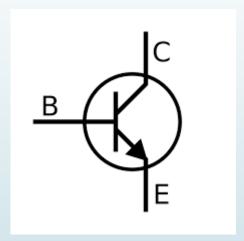A transistor contains a Base (B), Collector (C) and Emitter (E).



If a current flows on B it allows for a current to flow from C to E.


AND Gate

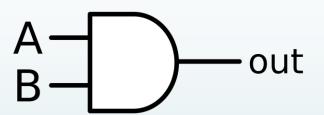


Α	В	Out	
0	0	0	
0	1	0	
1	0	0	
1	1	1	

0: 0V


1: 6V

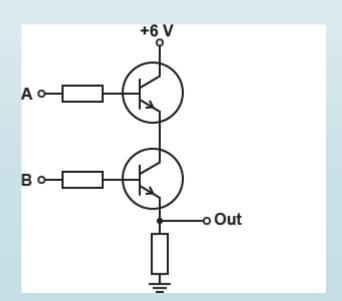


OR Gate

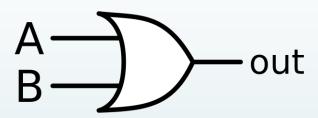


А	В	Out	
0	0	0	
0	1	1	
1	0	1	
1	1	1	

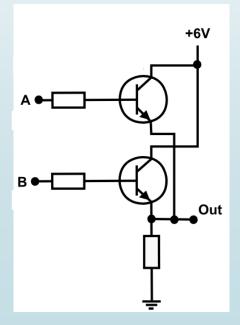


XOR Gate

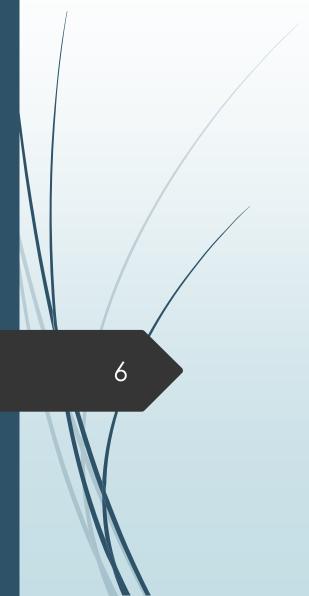

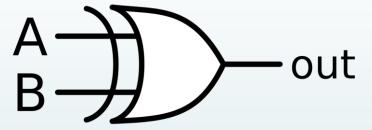


Α	В	Out	
0	0	0	
0	1	1	
1	0	1	
1	1	0	

Half adder circuit

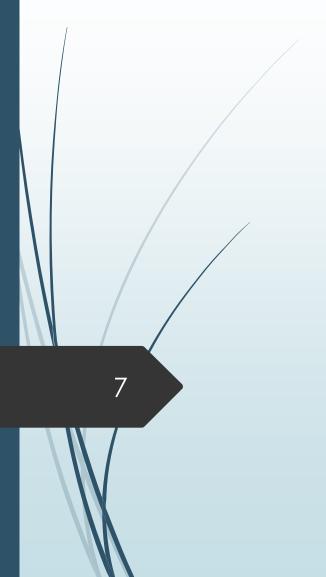

Α	В	S	С
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

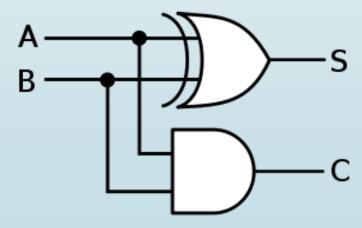

Software abstraction

Passage from a high-level language to a lower level language understood by the machine via several intermediate languages.


Human language X: read a video


Programmer language Y: load(video)

Binary language Z: 011...010

Conversion: $X \rightarrow \dots \rightarrow Y \rightarrow \dots \rightarrow Z$


Layers architecture

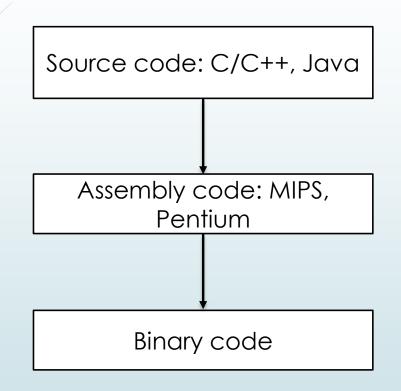

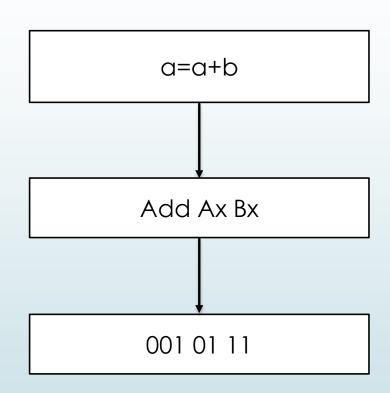

Ax and Bx are two registers (small memories)
Sub, Add, Mul, ... are mnemonics (functions)

Von Neuman machine

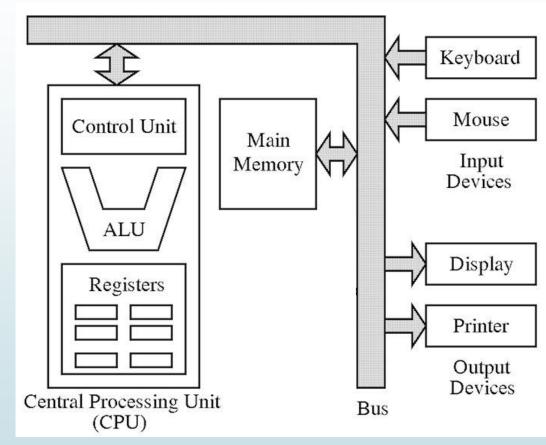

CPU: processor

10

Arithmetic and Logic Unit (ALU): permforms computation (+,-,*,/,...)

Register: a small memory that usually hols 32 or 64 bits (32-bit or 64-bit CPU).

Von Neuman machine

Three types of bus exist:

Control bus (unidirectional)




Address bus (unidirectional)



Data bus (bidirectional)

11



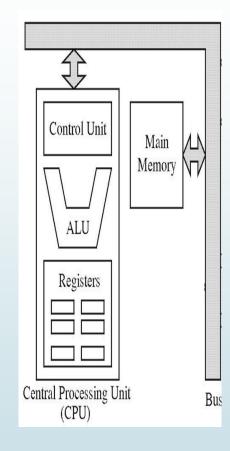

The control unit sends orders (read/write) via the control bus The control unit sends addresses via the address bus

CPU and Memory exchange data (information) via the data bus

Exercise

Consider the following machine:

- 2 control signals
- A RAM of 64 KB divided into cells of 2 bytes each

Q1: Determine the width of control and address buses.

Q2: Expalin how the machine executes z=x+y using the control, address and data buses, where x, y and z are located in adresses 10, 20, 30 respectively and have values 1, 5, 2 respectively.

